

# CCE1013 - Computer Logic 1

Giorgio Grigolo

B.Sc. Mathematics and Computer Science

Year 1, Semester 1 - 2021/22

## CONTENTS

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Proof of Correct Operation</b>	<b>2</b>
2.1	Opcode 00 - ADD . . . . .	2
2.1.1	Truth table . . . . .	2
2.1.2	Pictures . . . . .	3
2.2	Opcode 01 - ADDC . . . . .	7
2.2.1	Truth table . . . . .	7
2.2.2	Pictures . . . . .	8
2.3	Opcode 10 - SUB . . . . .	12
2.3.1	Truth table . . . . .	12
2.3.2	Pictures . . . . .	13
2.4	Opcode 11 - SUBB . . . . .	17
2.4.1	Truth table . . . . .	17
2.4.2	Pictures . . . . .	18

## INTRODUCTION

The following report indicates the operation of a 4-instruction arithmetic logic unit. The instructions are ADD, ADDC, SUB, SUBB represented by opcodes 00, 01, 10, 11 respectively. It is to be noted that this implementation of the above ALU outputs the  $C_o$  as the MSB by turning on the **red LED** (left) and outputs the  $Y$  as the LSB by turning on the **green LED** (right).

## PROOF OF CORRECT OPERATION

### 2.1 Opcode 00 - ADD


With this opcode selected, the ALU performs the addition of bits  $A$  and  $B$ , whilst ignoring the carry in represented by  $C_i$ .

$$A + B + 0 = C_o Y$$


#### 2.1.1 Truth table

$A$	$B$	$C_i$	$Op_1$	$Op_2$	$C_o$	$Y$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	0	1
1	0	0	0	0	0	1
1	0	1	0	0	0	1
1	1	0	0	0	1	0
1	1	1	0	0	1	0


### 2.1.2 Pictures

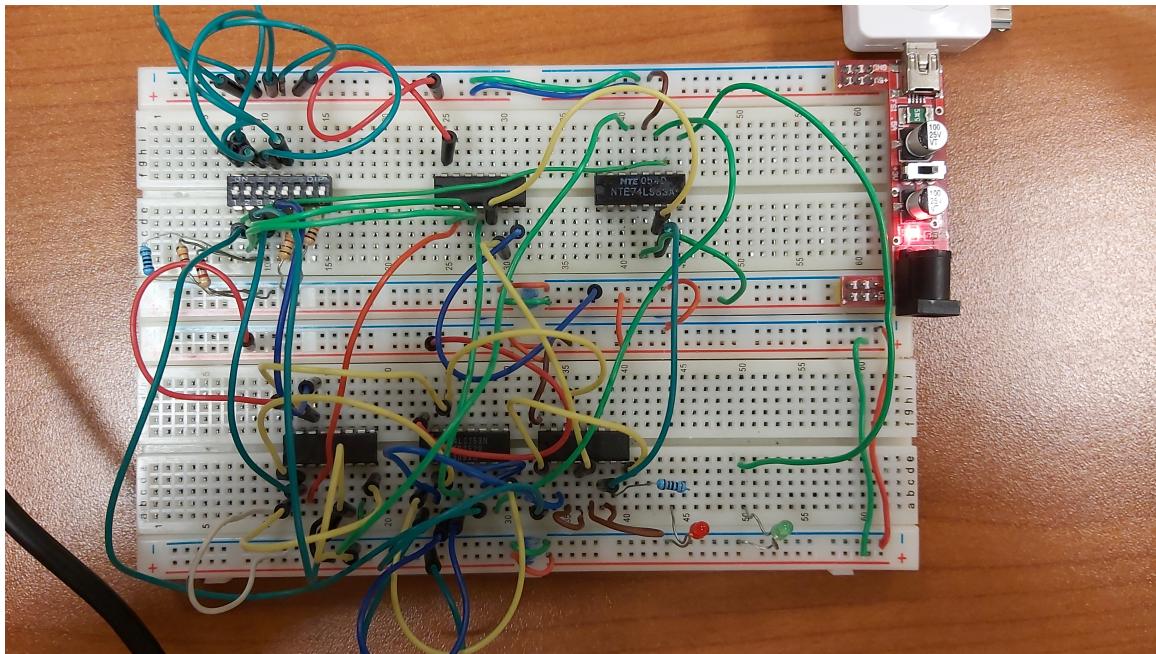

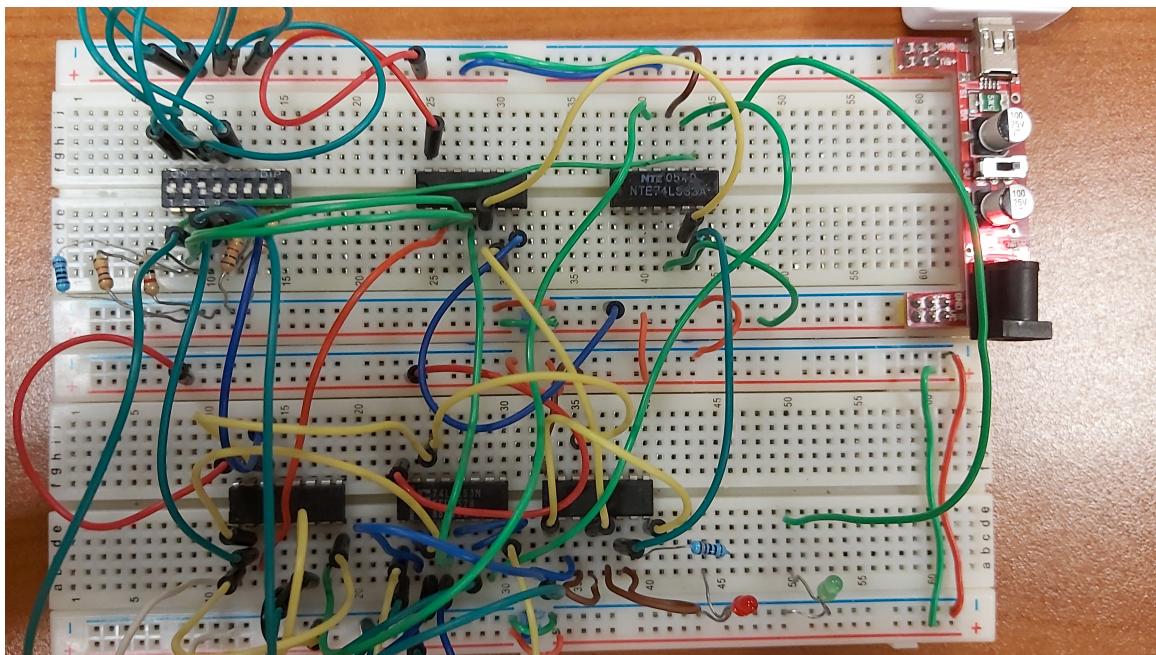
All inputs are off, and thus no LED is on.




$ABC_i = 001$  and so  $C_o Y = 00$ .

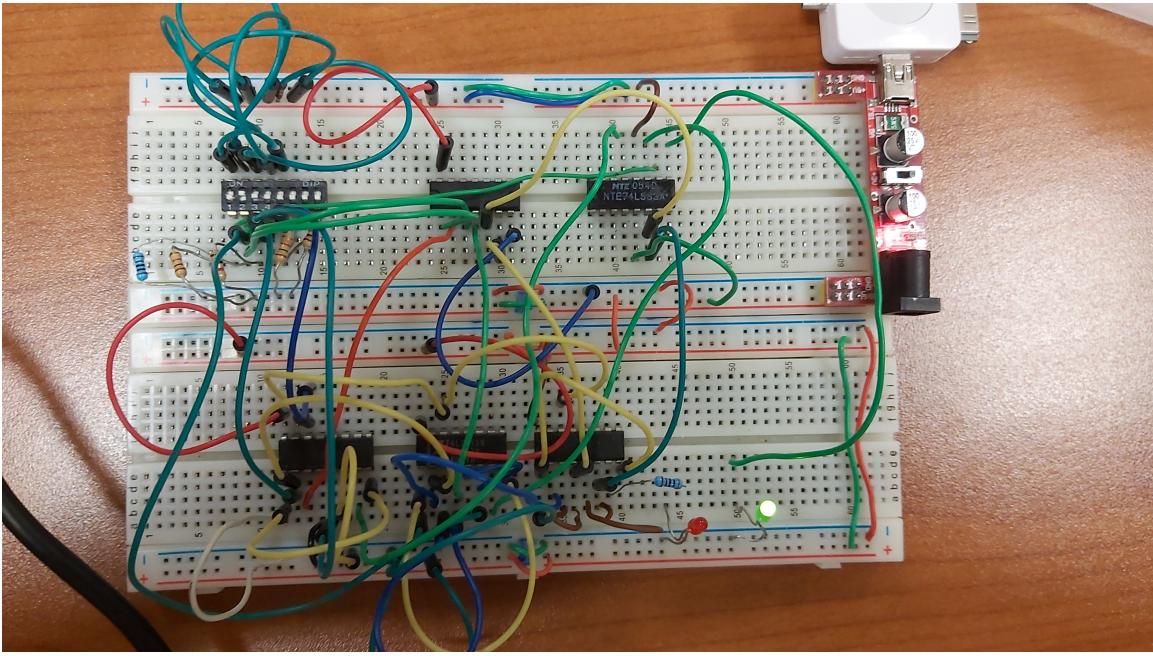


$ABC_i = 010$  and so  $C_oY = 01$ .

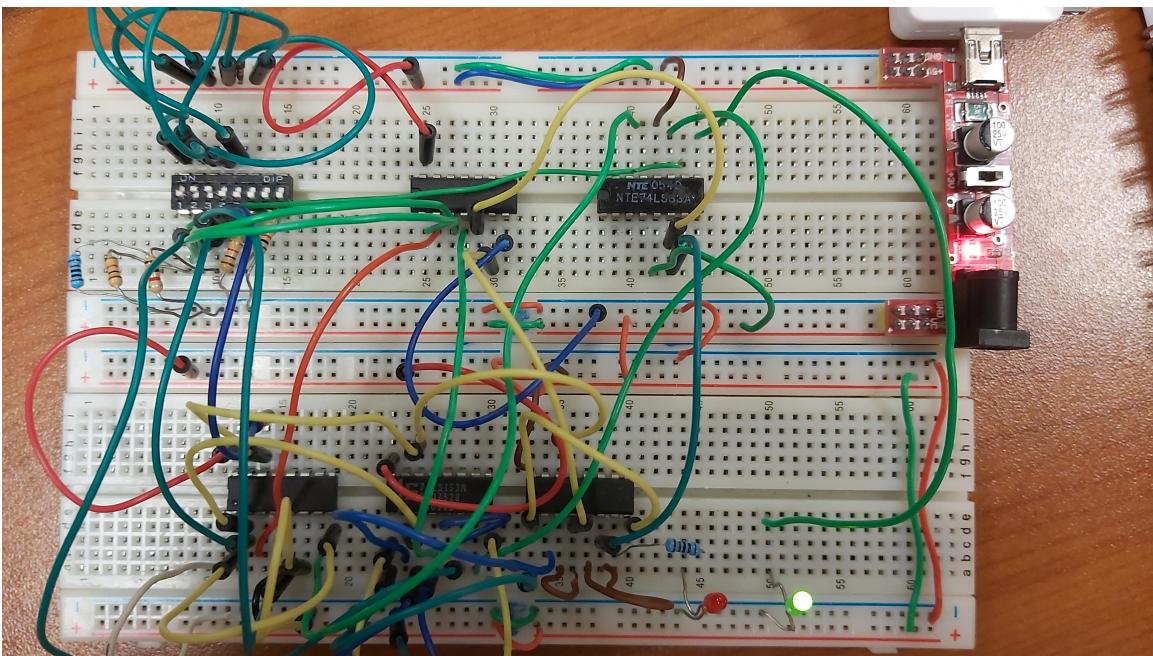


$ABC_i = 011$  and so  $C_oY = 01$ .

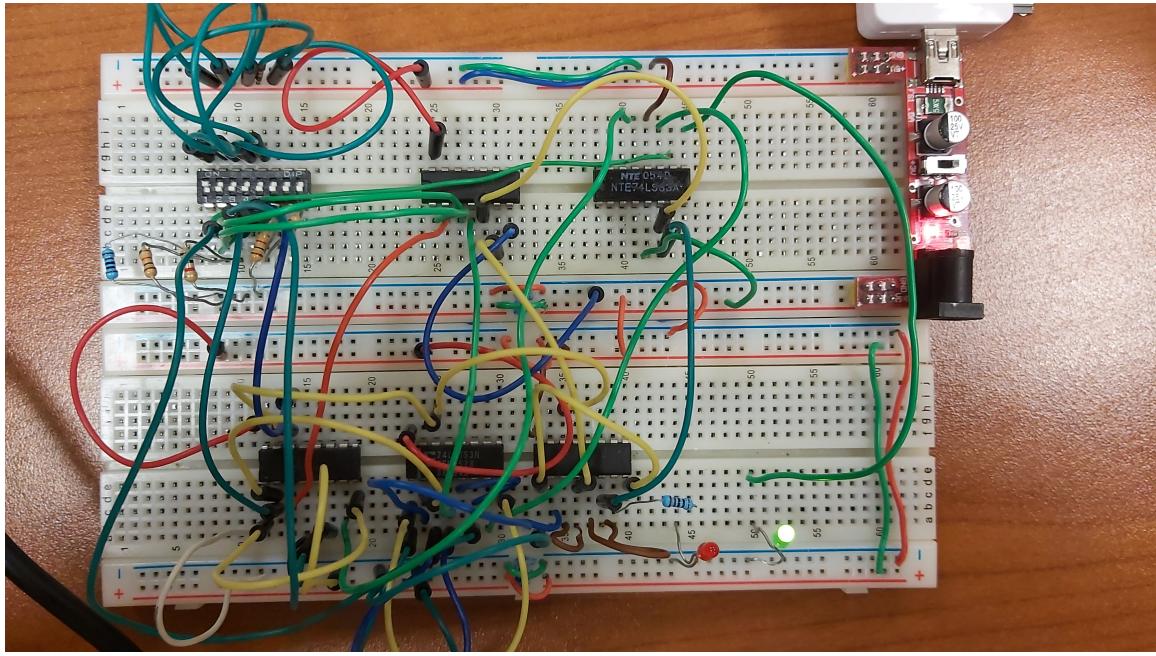


$ABC_i = 100$  and so  $C_oY = 01$ .

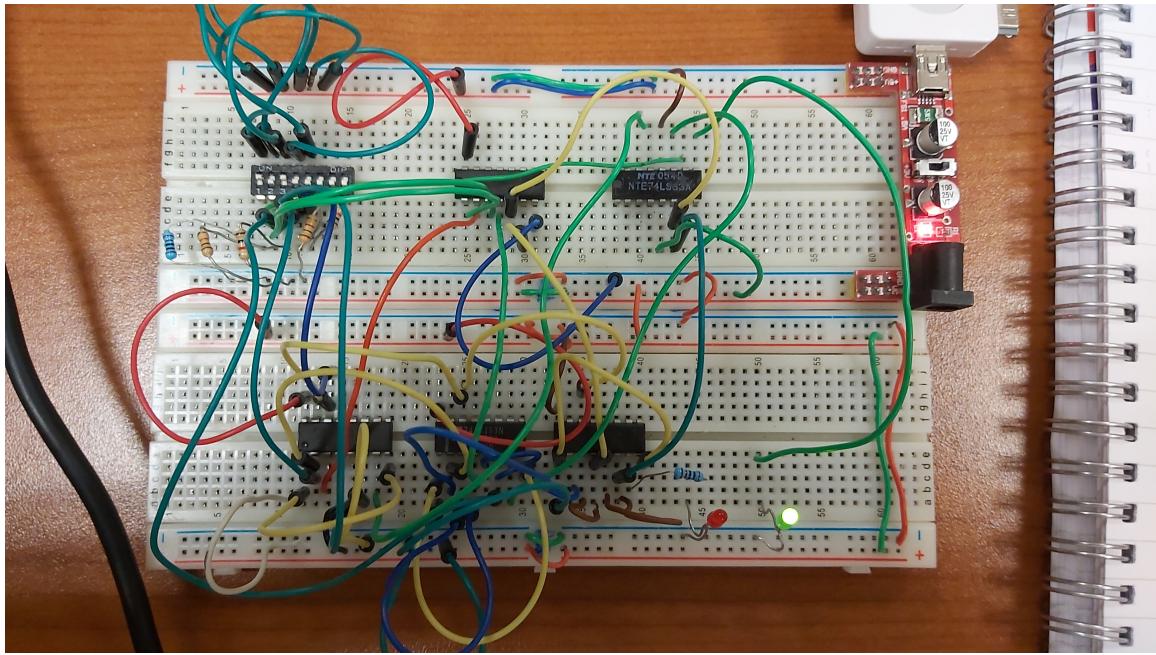

$ABC_i = 101$  and so  $C_oY = 01$ .

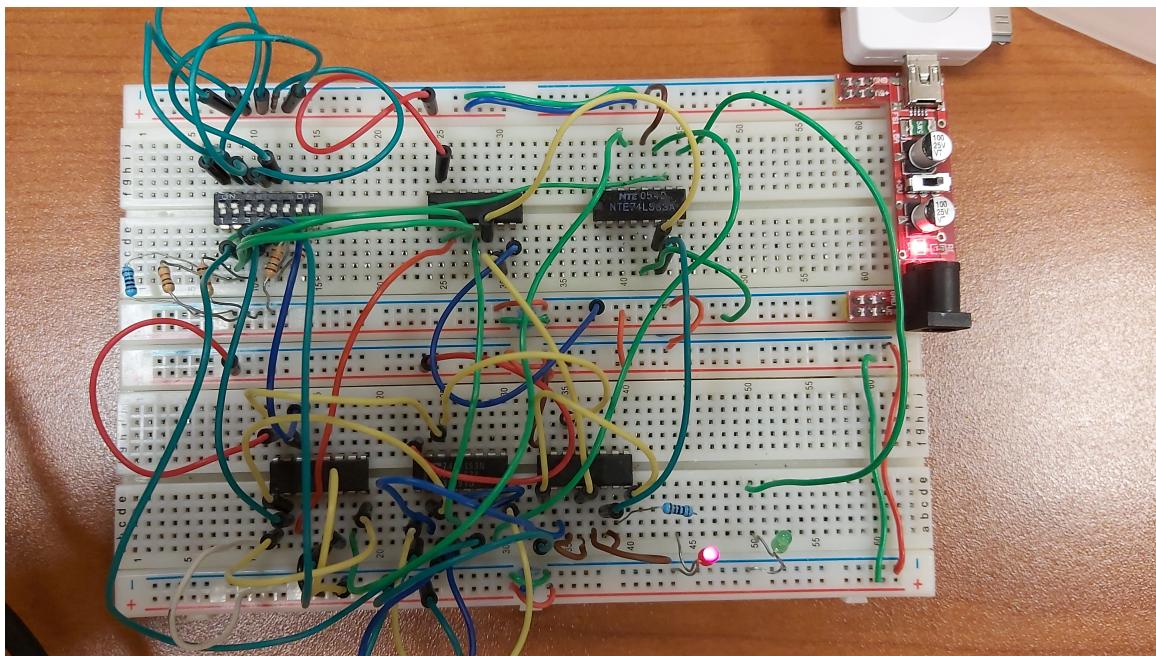
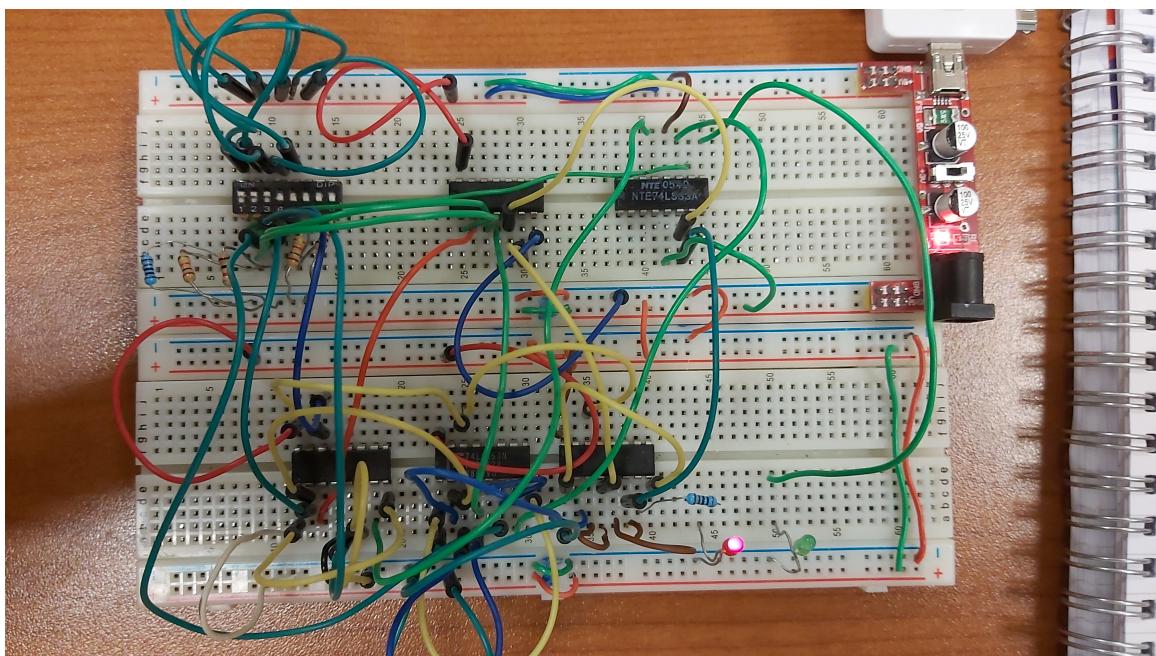
$$ABC_i = 110 \text{ and so } C_o Y = 10.$$



$$ABC_i = 111 \text{ and so } C_o Y = 10.$$

## 2.2 Opcode 01 – ADDC


With this opcode selected, the ALU performs the addition of bits  $A$  and  $B$  but consequently adding the carry bit represented by  $C_i$ .

$$A + B + C_i = C_o Y$$


### 2.2.1 Truth table

$A$	$B$	$C_i$	$Op_1$	$Op_2$	$C_o$	$Y$
0	0	0	0	1	0	0
0	0	1	0	1	0	0
0	1	0	0	1	0	1
0	1	1	0	1	0	1
1	0	0	0	1	0	1
1	0	1	0	1	0	1
1	1	0	0	1	1	0
1	1	1	0	1	1	0


## 2.2.2 Pictures

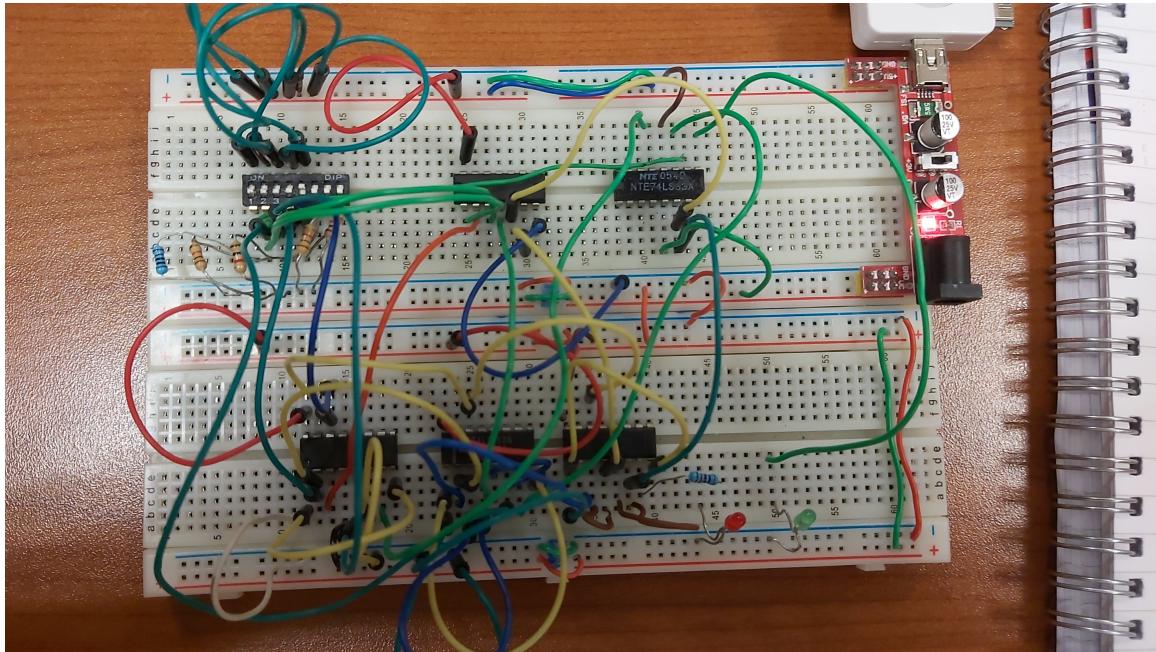

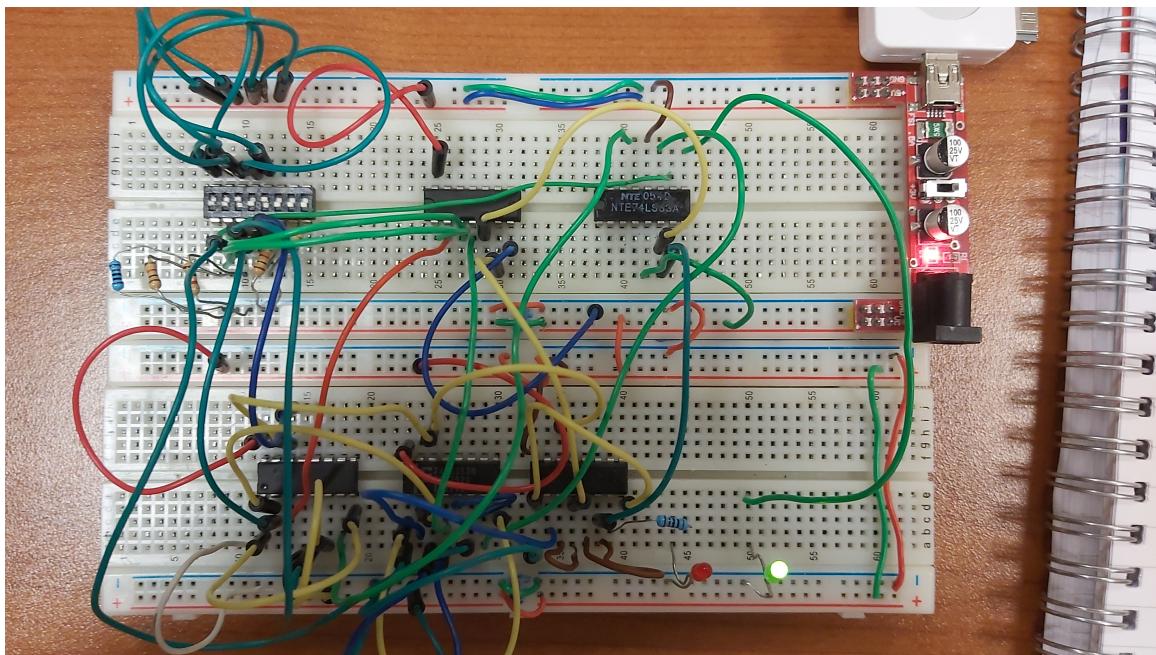
All inputs are off, and thus no LED is on.




$ABC_i = 001$  and so  $C_o Y = 01$ .

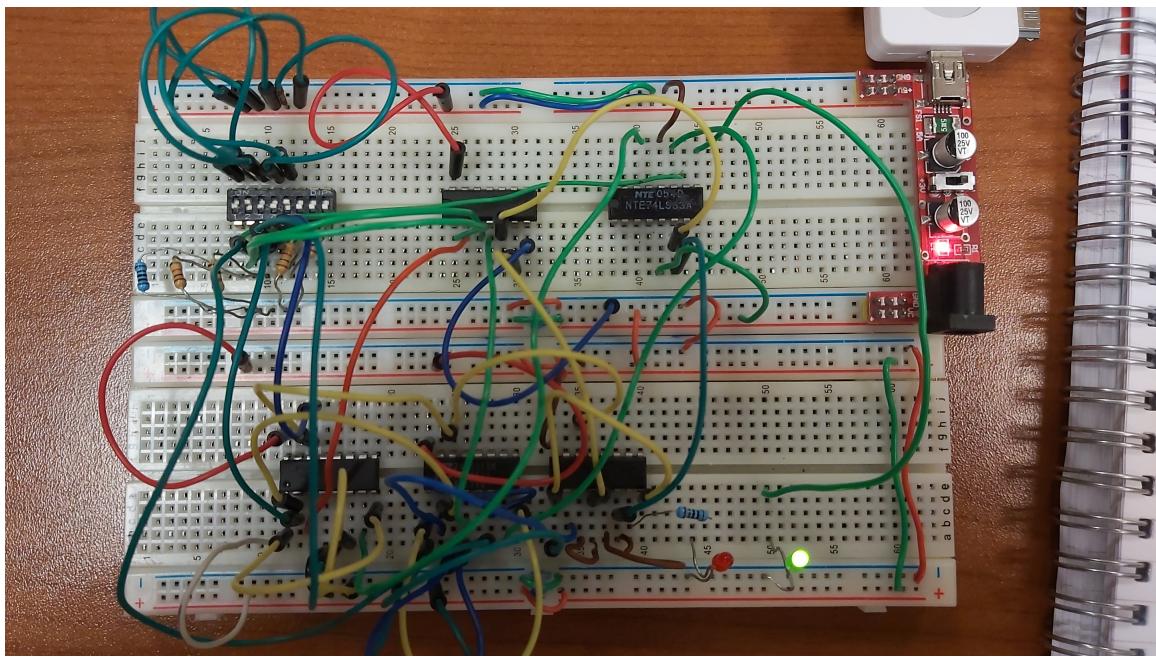


$ABC_i = 010$  and so  $C_oY = 01$ .

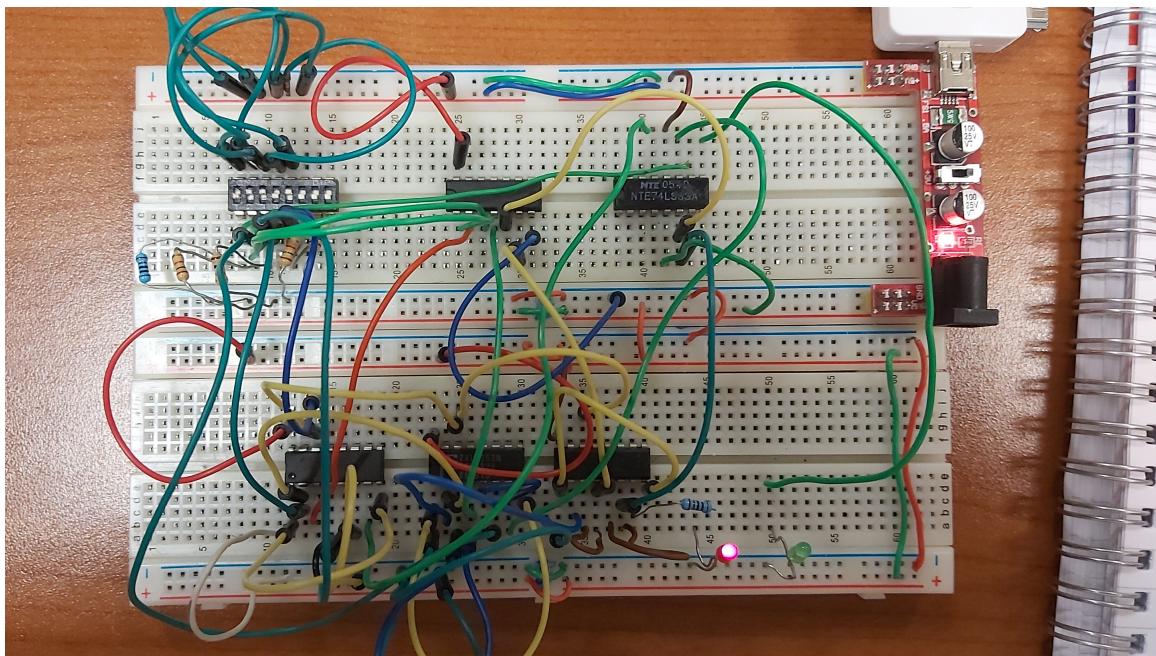


$ABC_i = 011$  and so  $C_oY = 10$ .

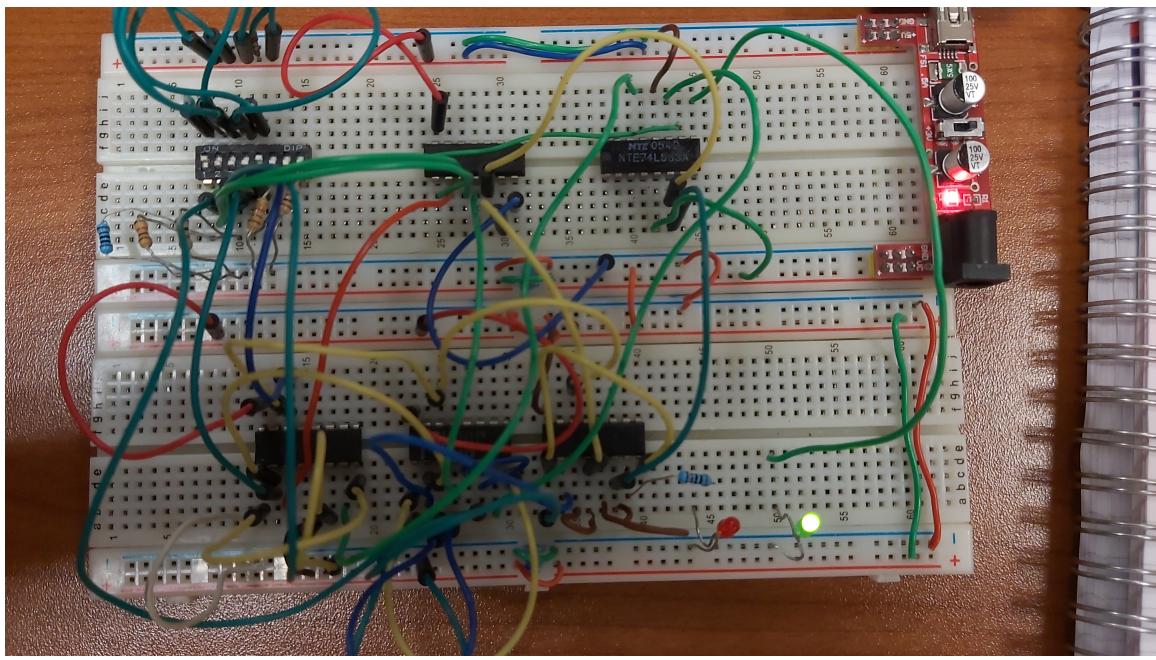


$ABC_i = 100$  and so  $C_oY = 01$ .

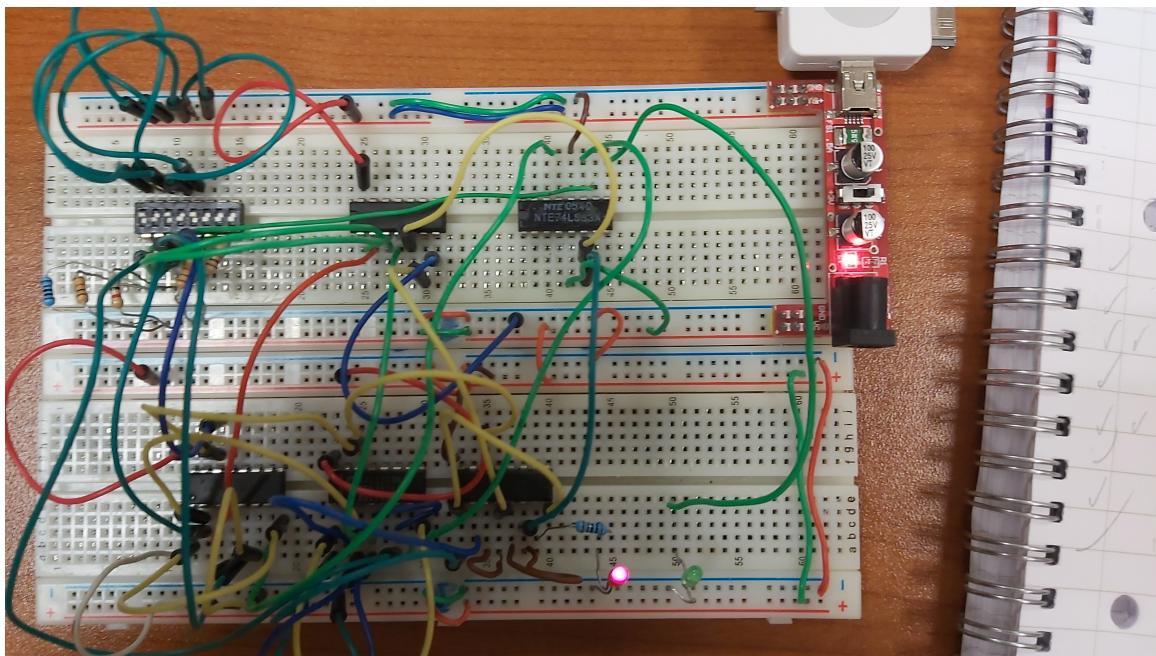

$ABC_i = 101$  and so  $C_oY = 10$ .

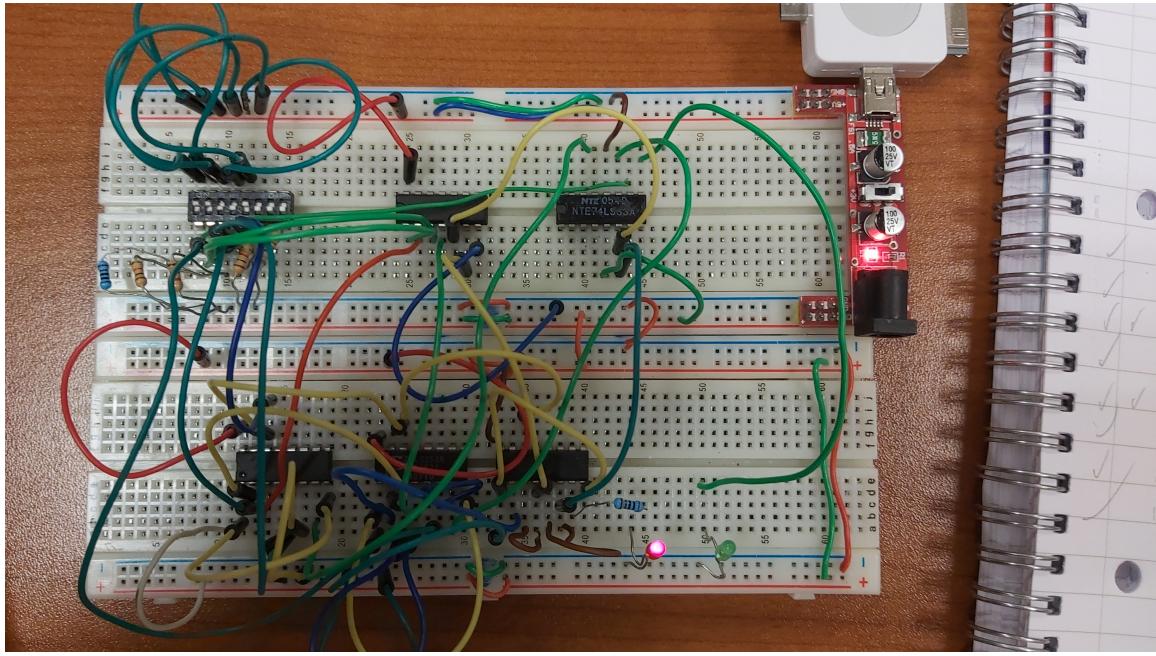

$ABC_i = 110$  and so  $C_oY = 10$ .

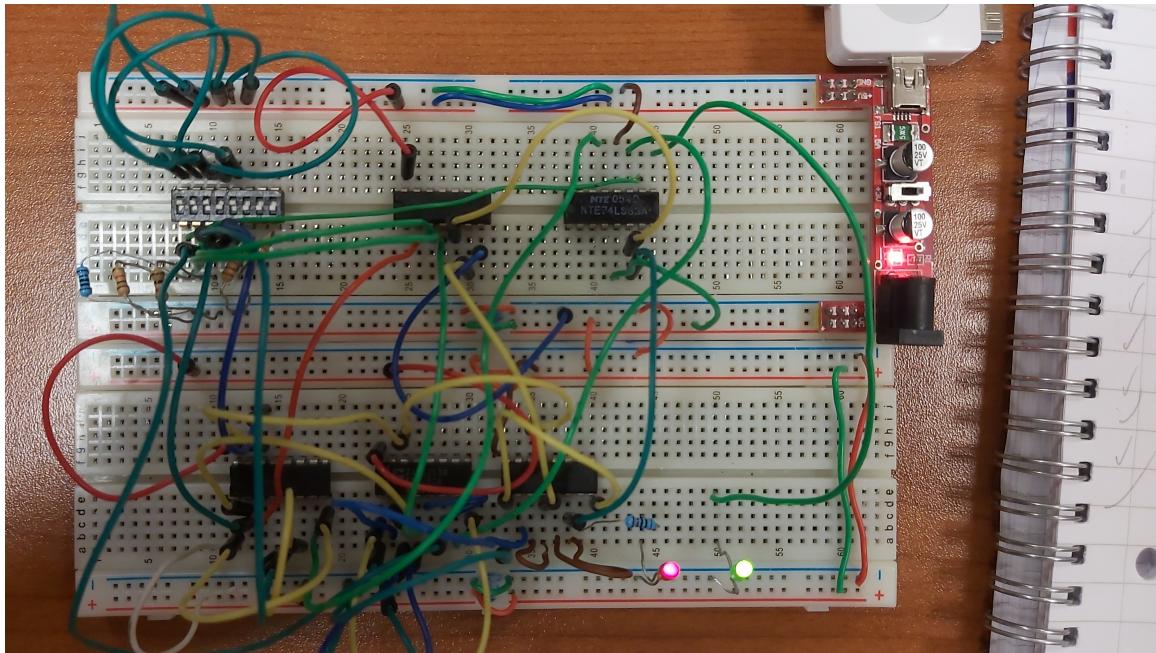

$ABC_i = 111$  and so  $C_oY = 11$ .

### 2.3 Opcode 10 – SUB


With this opcode selected, the ALU performs the subtraction of bits  $A$  and  $B$ , or rather, the addition of  $A$ ,  $\bar{B}$  and 1, whilst ignoring the borrow bit  $C_i$ . When a negative value is obtained, the resultant representation will be one in 2's complement, and so  $-1_{10}$  would be represented as  $11_2 = -2_{10} + 1_{10}$ .

$$A + \bar{B} + 1 = C_o Y$$


#### 2.3.1 Truth table

$A$	$B$	$C_i$	$Op_1$	$Op_2$	$C_o$	$Y$
0	0	0	1	0	0	0
0	0	1	1	0	0	0
0	1	0	1	0	1	1
0	1	1	1	0	0	0
1	0	0	1	0	0	1
1	0	1	1	0	0	1
1	1	0	1	0	0	0
1	1	1	1	0	0	0


### 2.3.2 Pictures

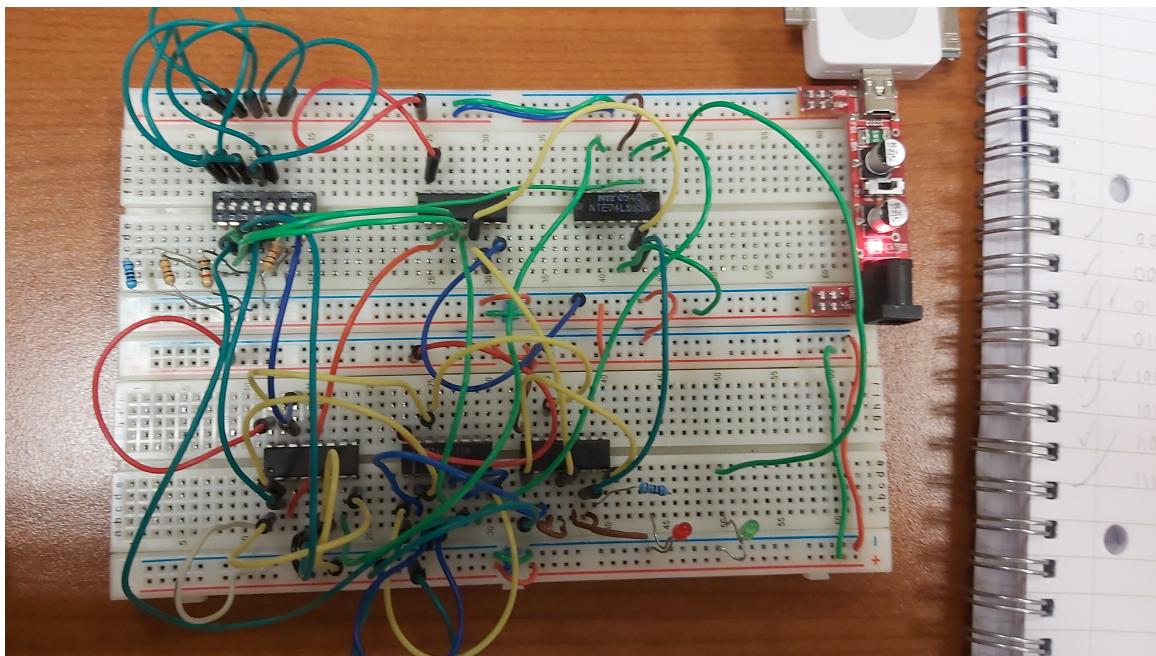

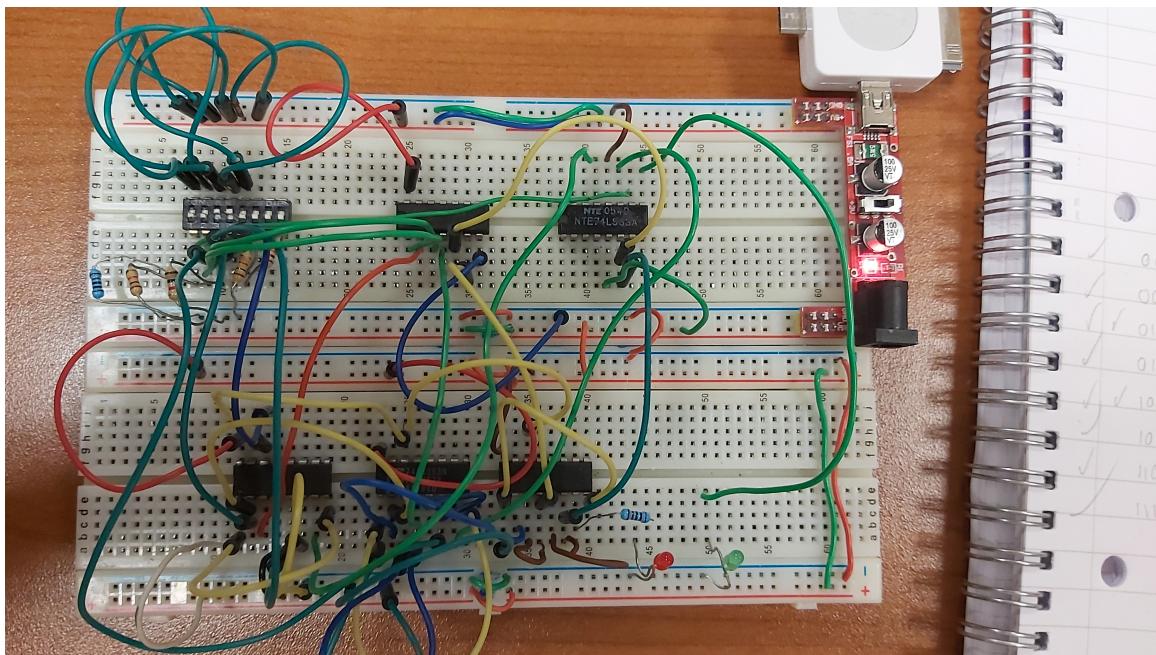
All inputs are off, and thus no LED is on.




$ABC_i = 001$  and so  $C_o Y = 00$ .

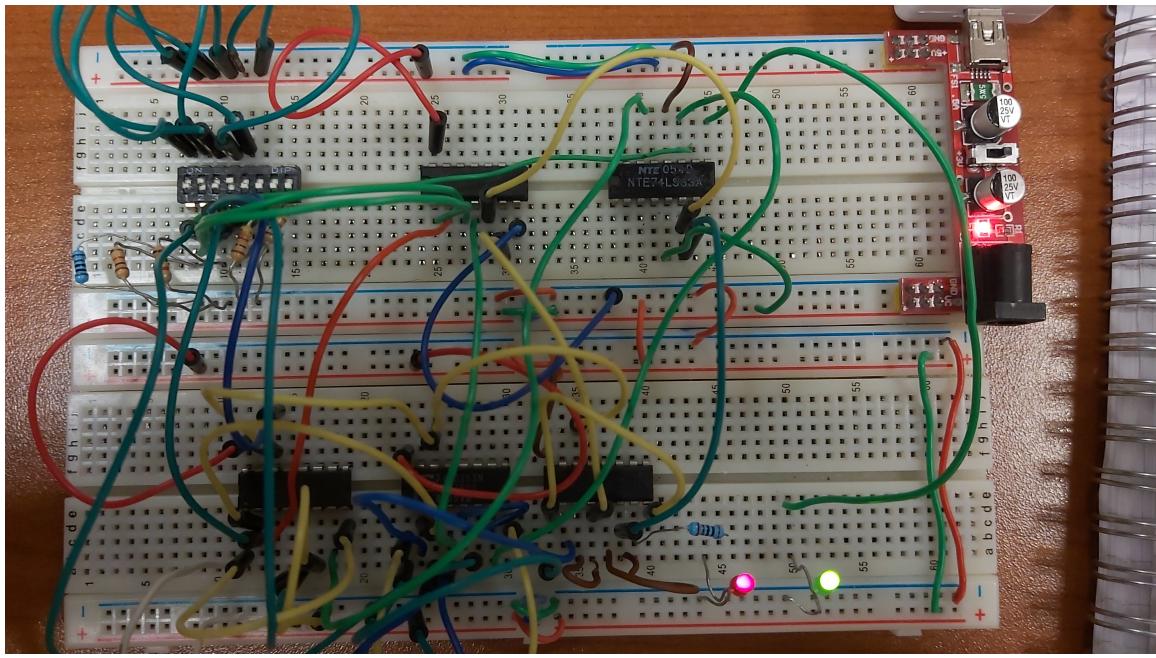


$ABC_i = 010$  and so  $C_oY = 11$ .

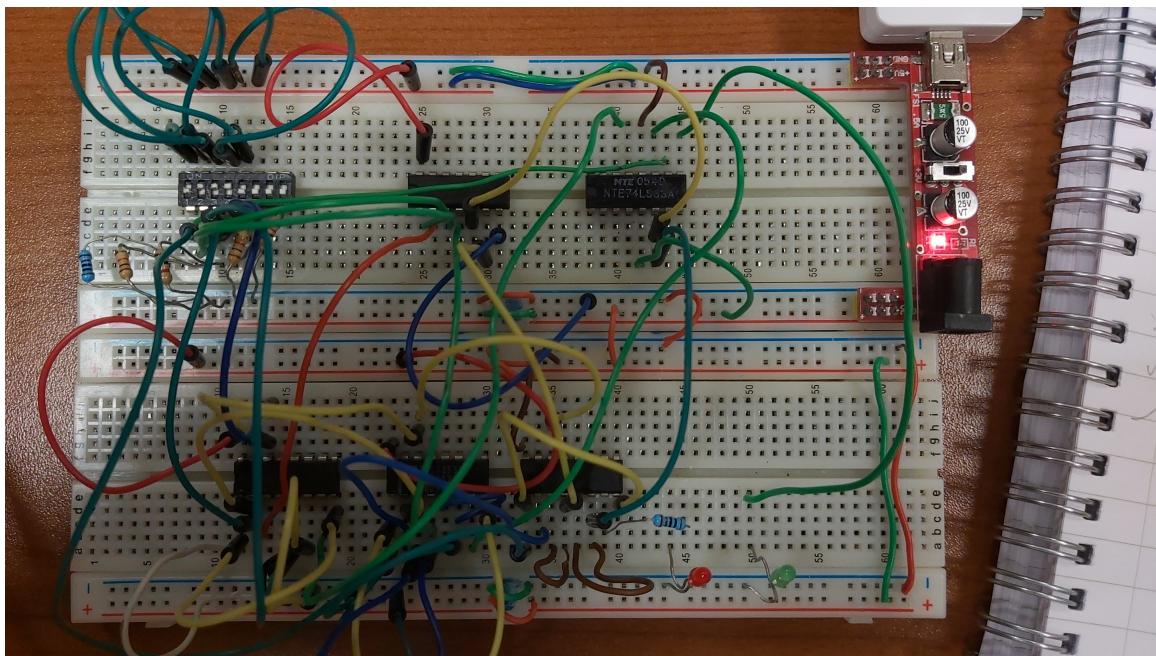


$ABC_i = 011$  and so  $C_oY = 00$ .

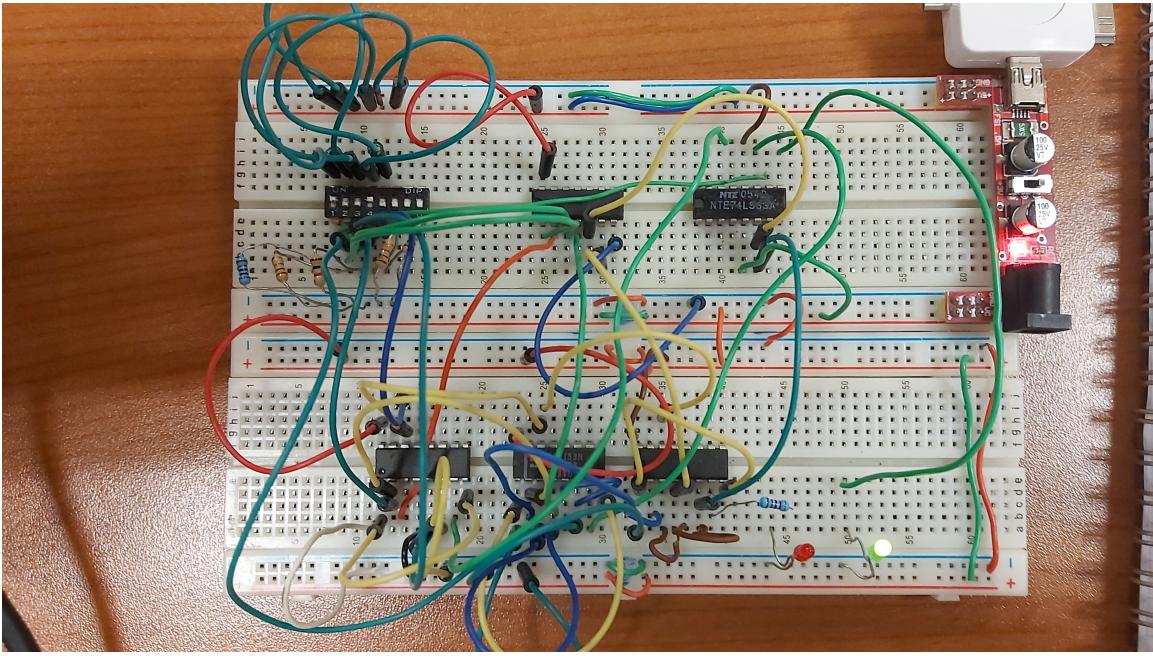


$ABC_i = 100$  and so  $C_oY = 01$ .

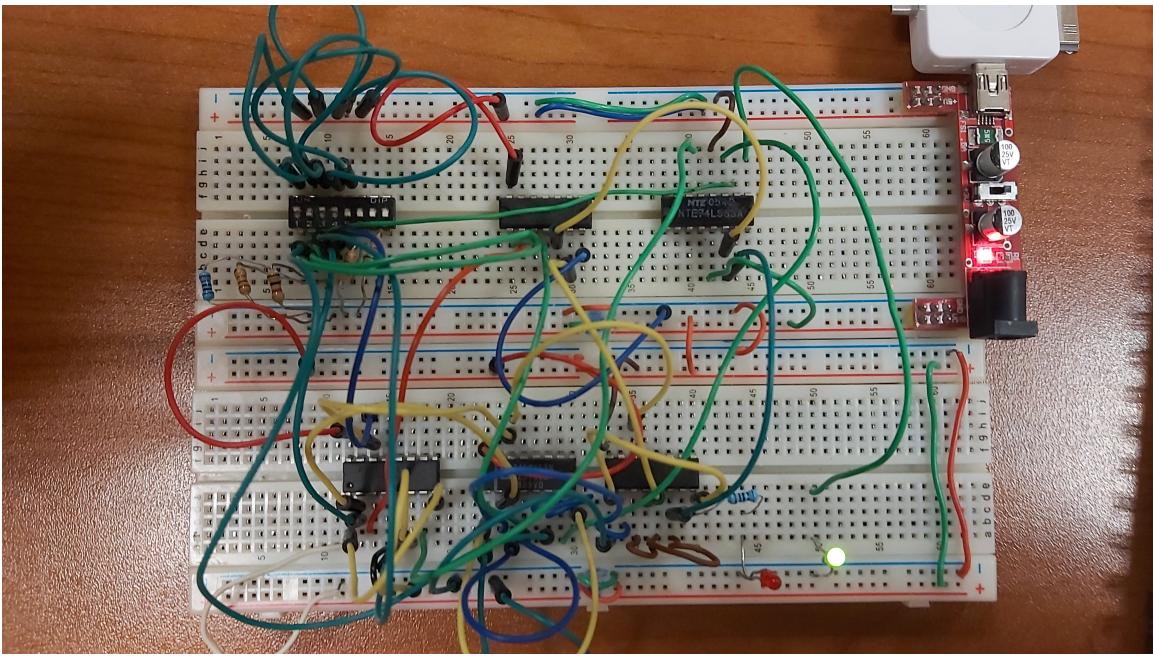

$ABC_i = 101$  and so  $C_oY = 01$ .

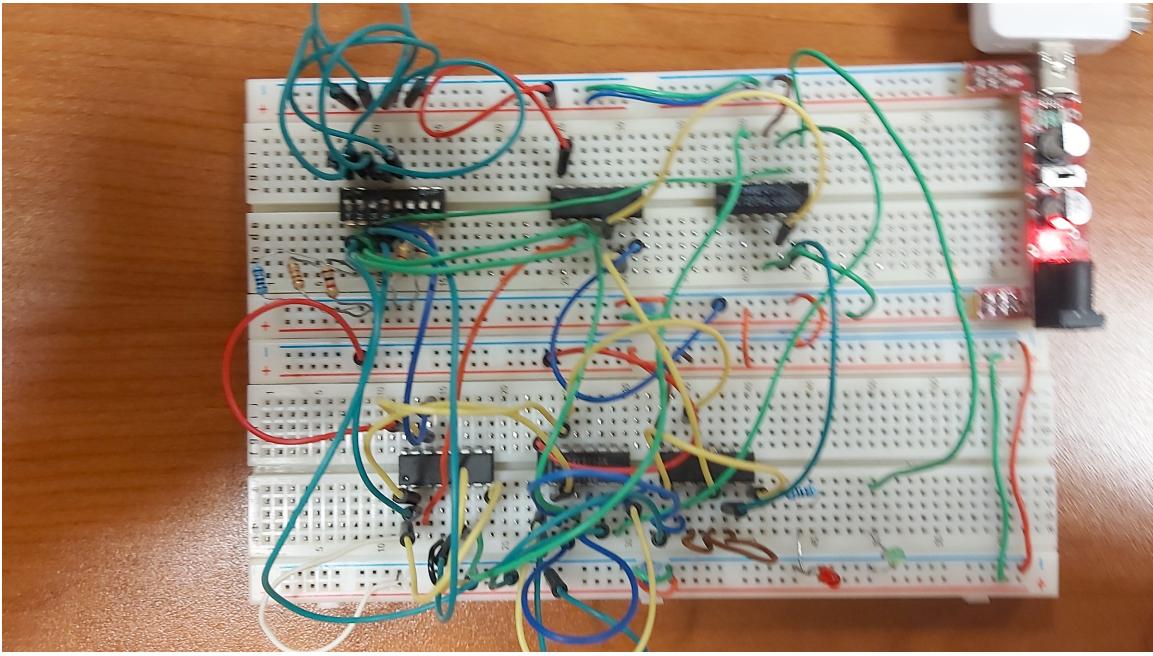

$ABC_i = 110$  and so  $C_o Y = 00$ .

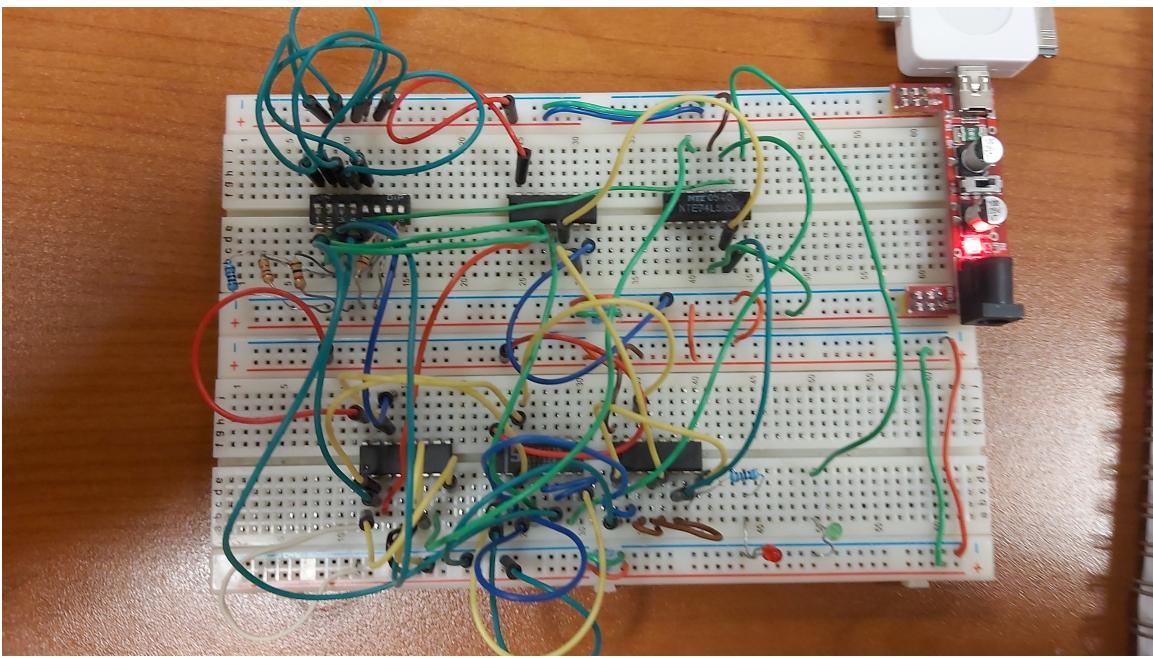

$ABC_i = 111$  and so  $C_o Y = 00$ .

## 2.4 Opcode 11 – SUBB


With this opcode selected, the ALU performs the subtraction of bits  $A$  and  $B$ , or rather, the addition of  $A$  and  $\bar{B}$ , whilst ignoring the borrow bit  $C_i$ . When a negative value is obtained, the resultant representation will be one in 2's complement, and so  $-1_{10}$  would be represented as  $11_2 = -2_{10} + 1_{10}$ .

$$A + \bar{B} + \bar{C}_i = C_o Y$$


### 2.4.1 Truth table

$A$	$B$	$C_i$	$Op_1$	$Op_2$	$C_o$	$Y$
0	0	0	1	1	0	0
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	0
1	0	0	1	1	0	1
1	0	1	1	1	0	0
1	1	0	1	1	0	0
1	1	1	1	1	1	1


## 2.4.2 Pictures

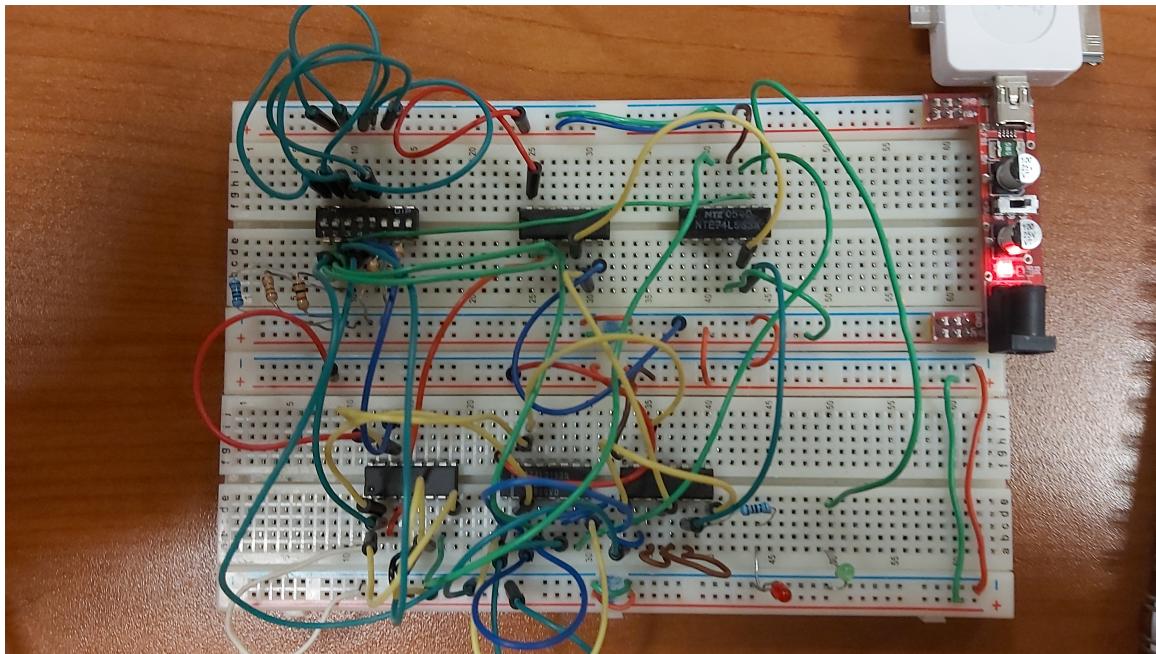

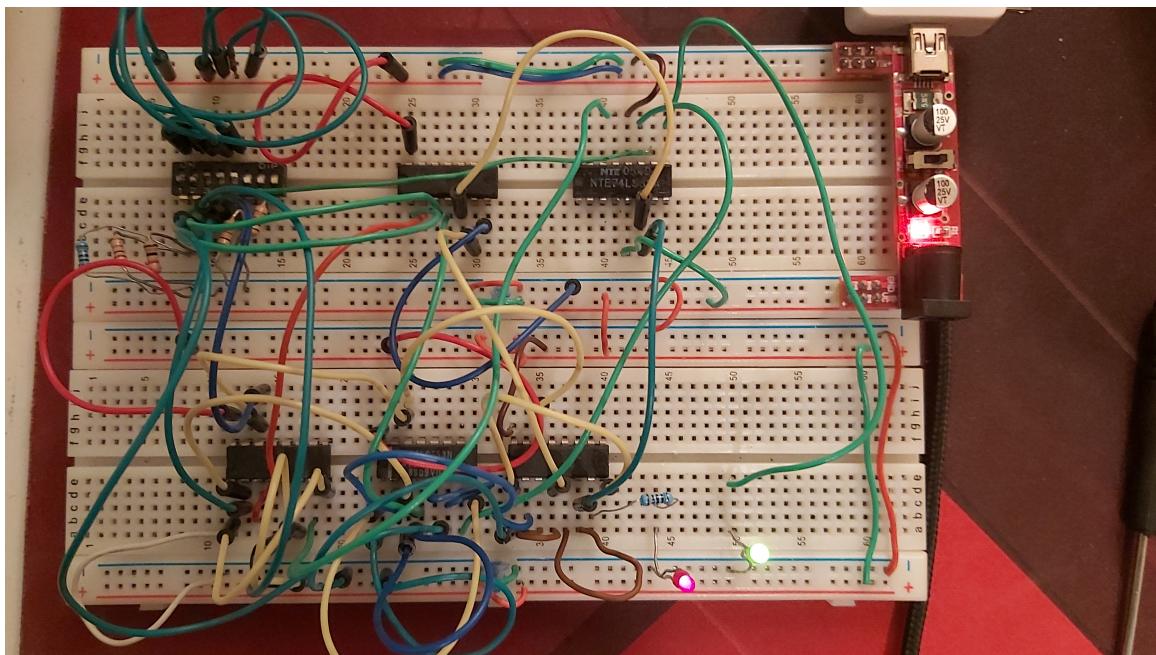
All inputs are off, and thus no LED is on.




$ABC_i = 001$  and so  $C_o Y = 11$ .

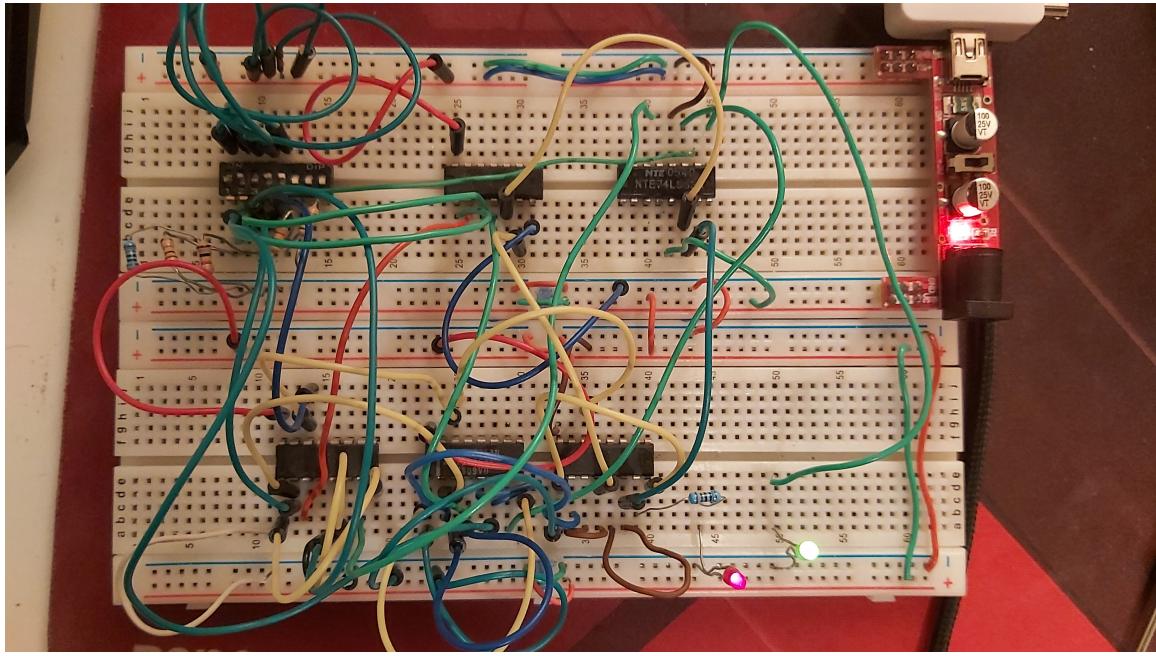


$ABC_i = 010$  and so  $C_oY = 11$ .

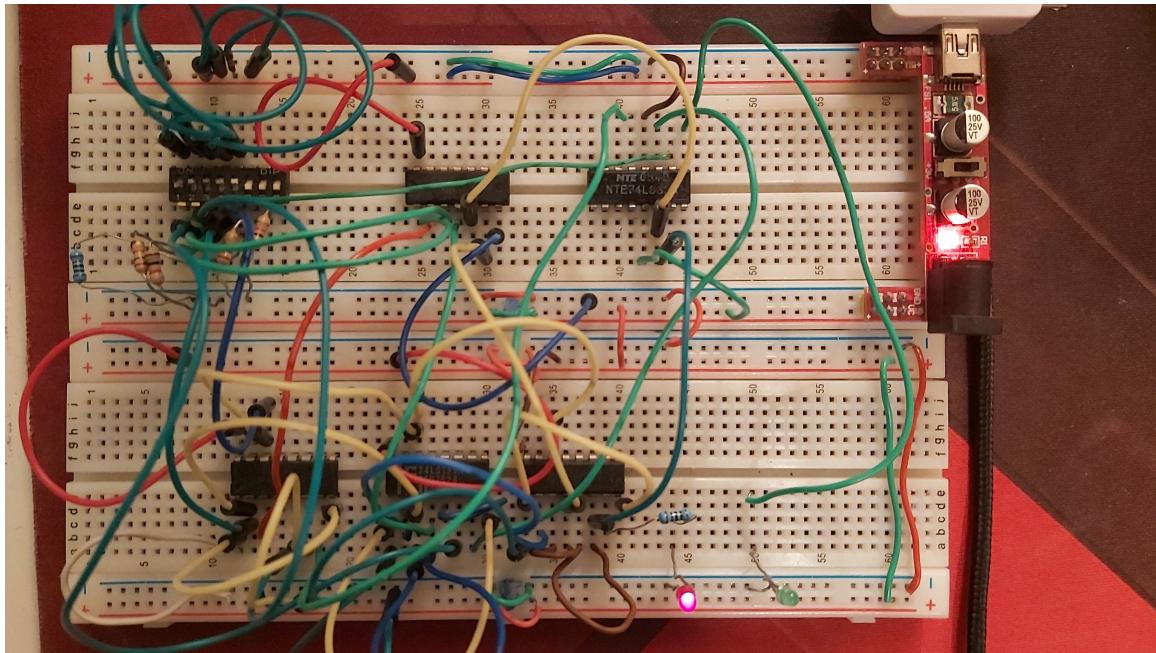


$ABC_i = 011$  and so  $C_oY = 10$ .

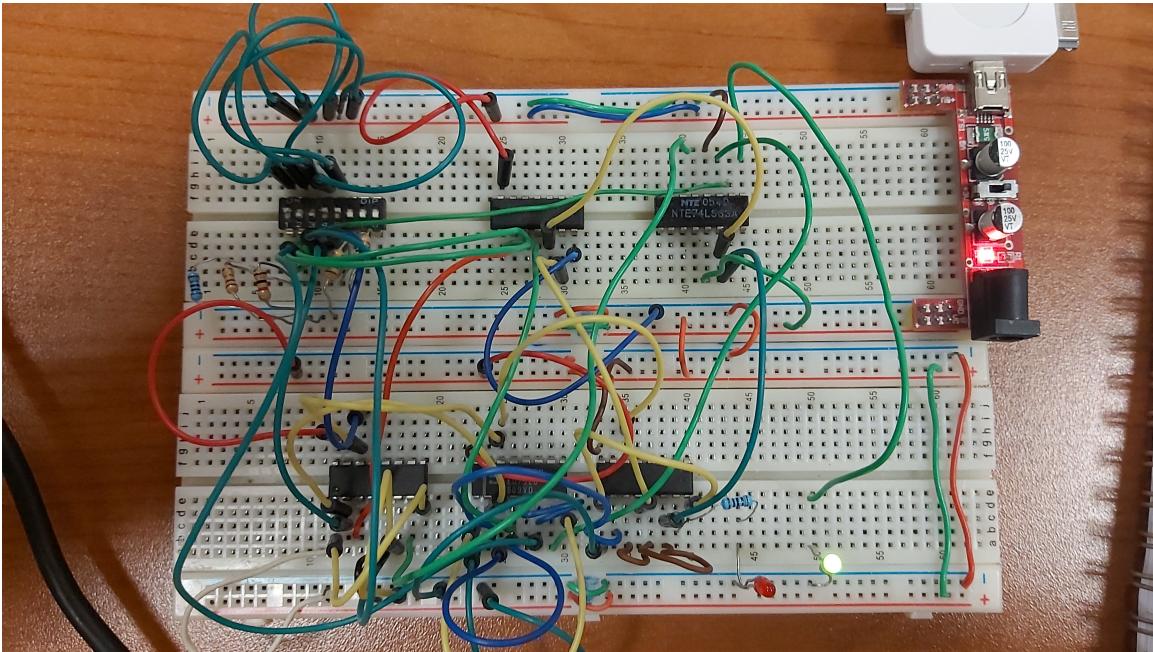


$ABC_i = 100$  and so  $C_oY = 01$ .

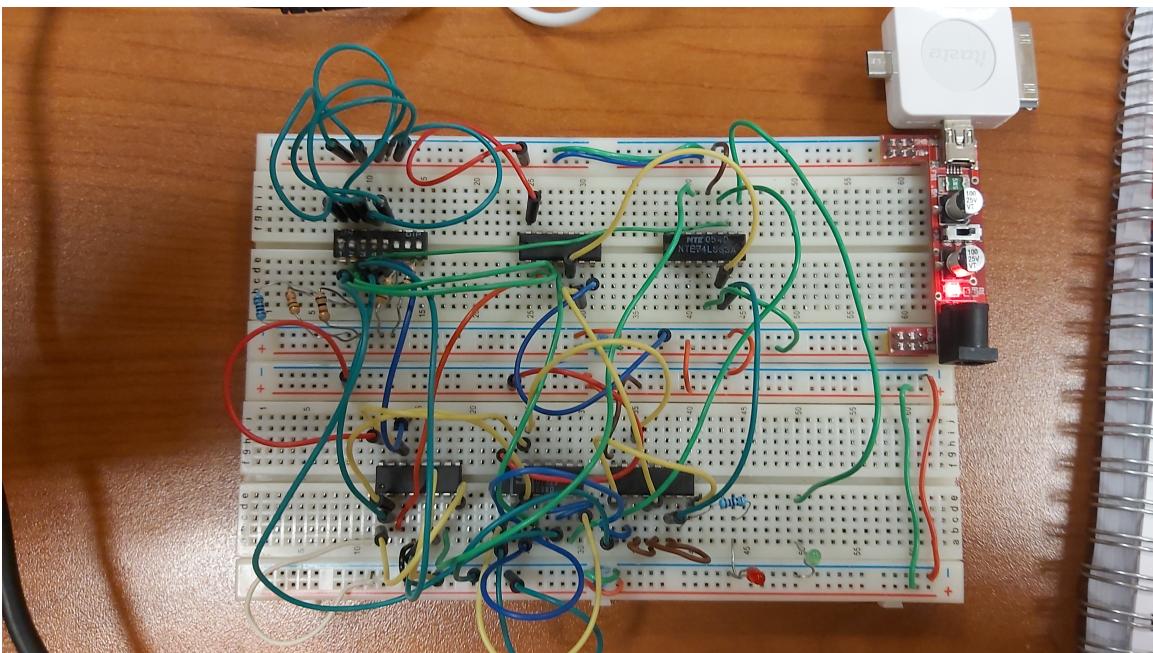

$ABC_i = 101$  and so  $C_oY = 00$ .

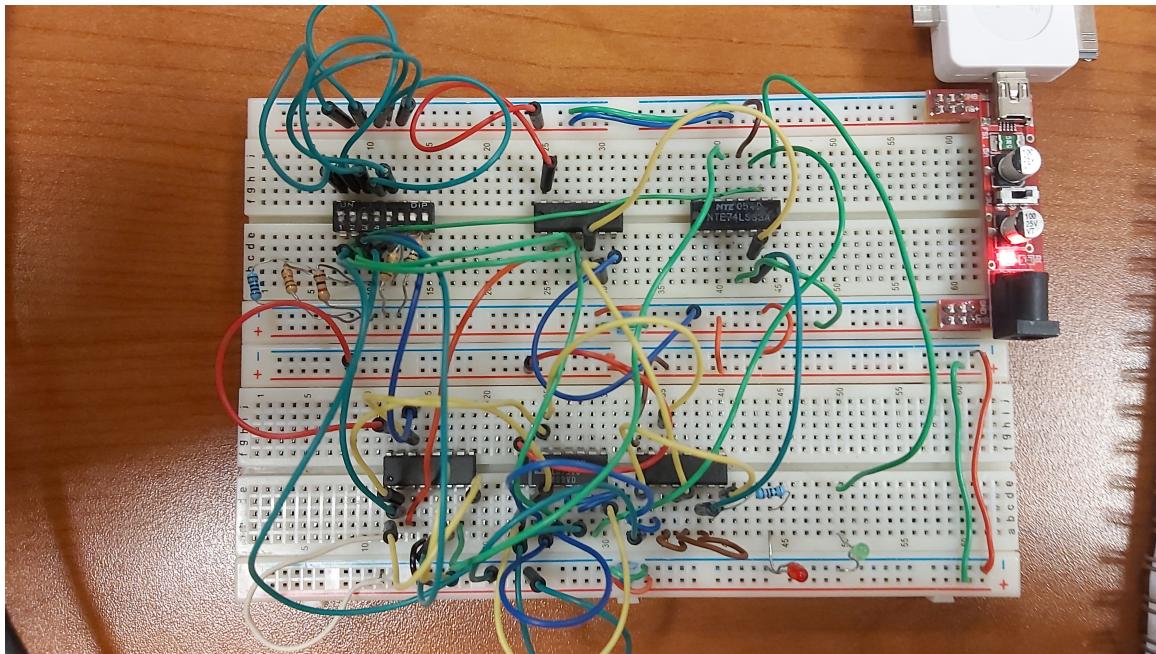

$ABC_i = 110$  and so  $C_oY = 00$ .

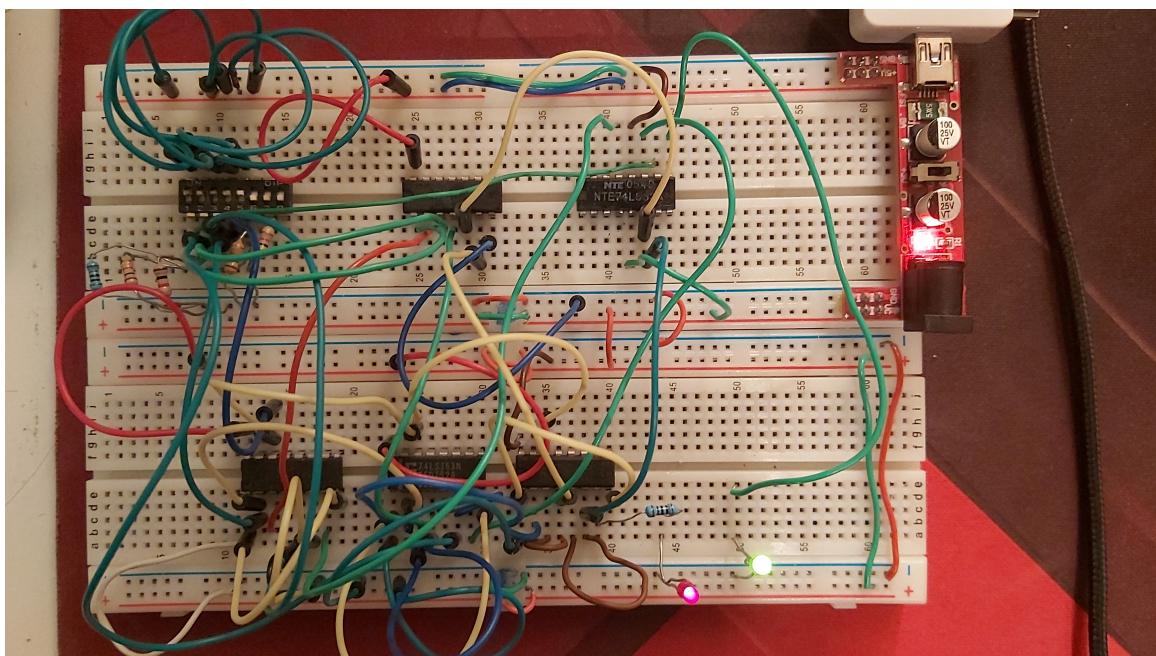

$ABC_i = 111$  and so  $C_oY = 11$ .